

Electrical Science

EIT Review

Session 1

Sources

Resistor, Ohm's Law

KVL, KCL

Node Analysis

Mesh Analysis

Power

Resistor combinations


Thevenin equivalents

Inductor


Capacitor

Transients

Independent Sources

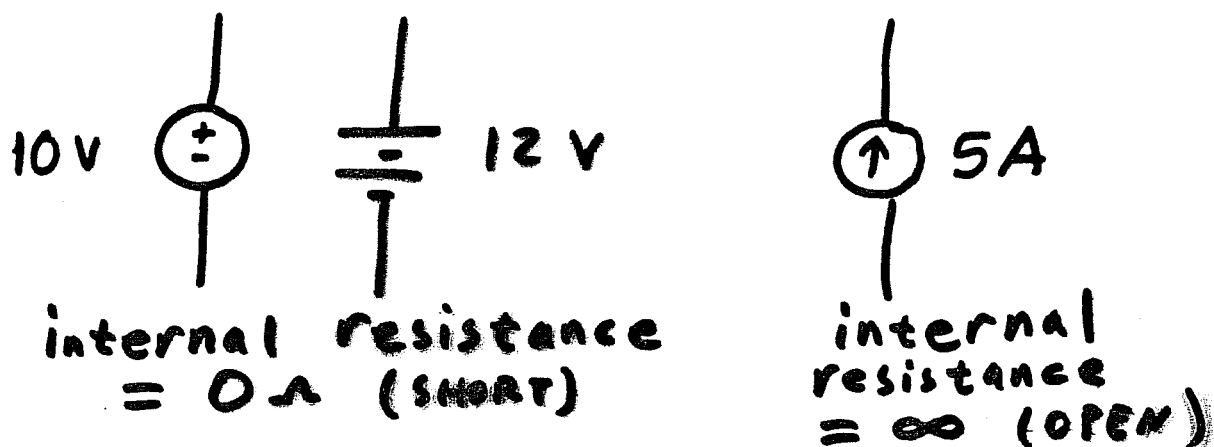

Dependent Sources

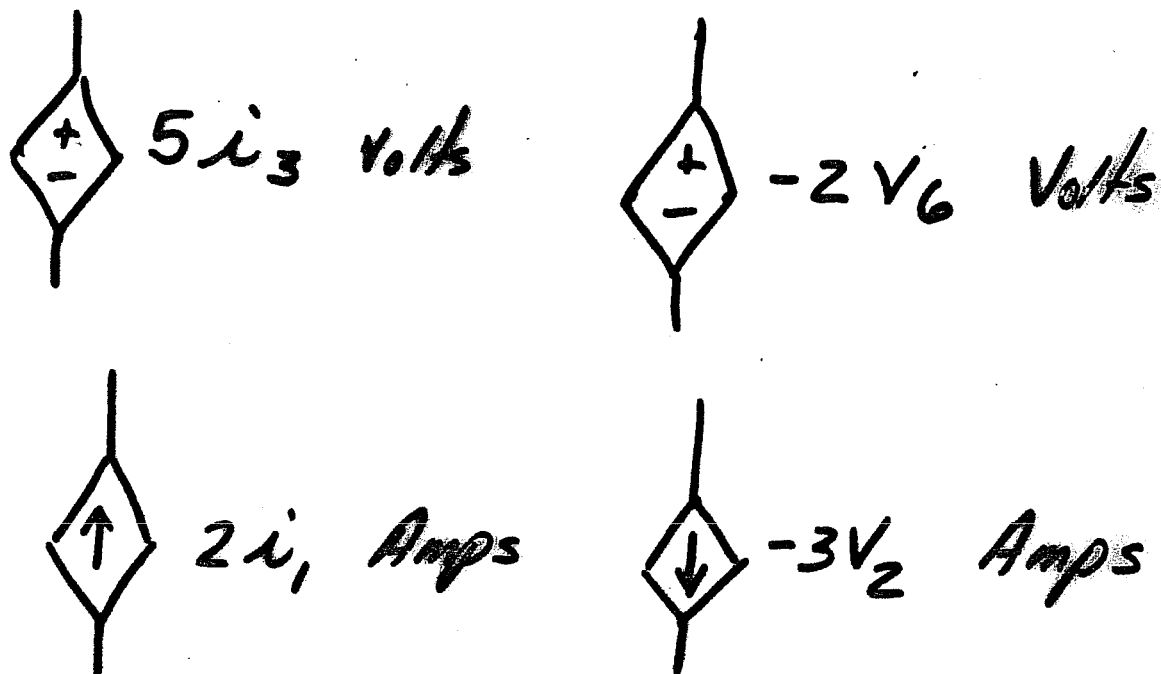

The Resistor




$$I = V/R \quad (\text{Ohm's Law})$$

Assume current enters positive terminal. Then

$$\begin{aligned}
 \underline{P}_{\text{absorbed}} &= V \cdot I \\
 &= \frac{V^2}{R} \\
 &= I^2 R
 \end{aligned}$$

Kirchoff's Voltage Law

\sum Voltages around
any closed path = 0

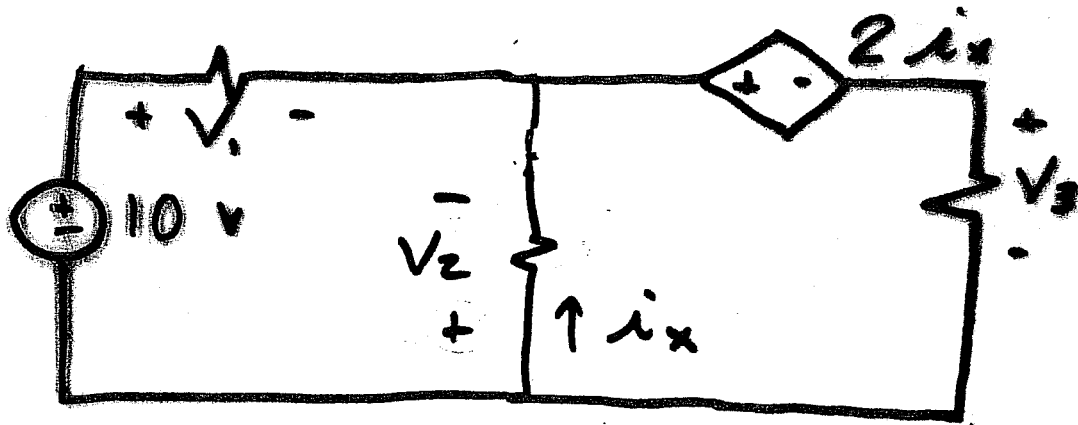


$$-10 + V_1 - V_2 = 0$$

$$-10 + V_1 + 2i_x + V_3 = 0$$

$$+V_2 + 2i_x + V_3 = 0$$

Kirchoff's Current Law

\sum currents into
a node = 0

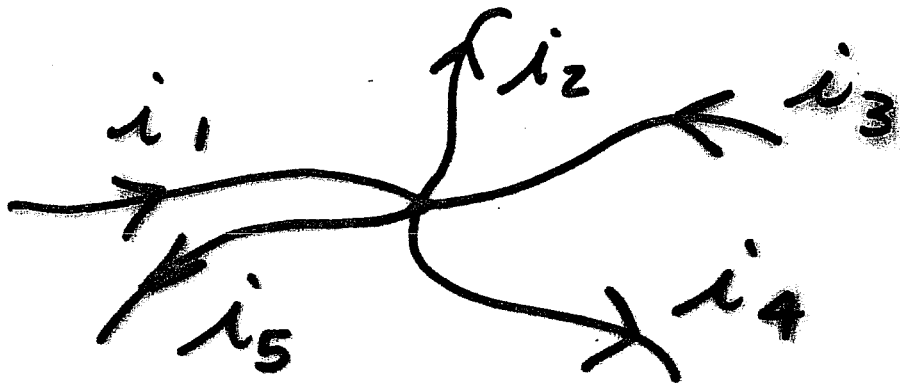


$$i_1 - i_2 + i_3 - i_4 - i_5 = 0$$

$$i_1 + i_3 = i_2 + i_4 + i_5$$

(incoming) = (leaving)

Nodal analysis

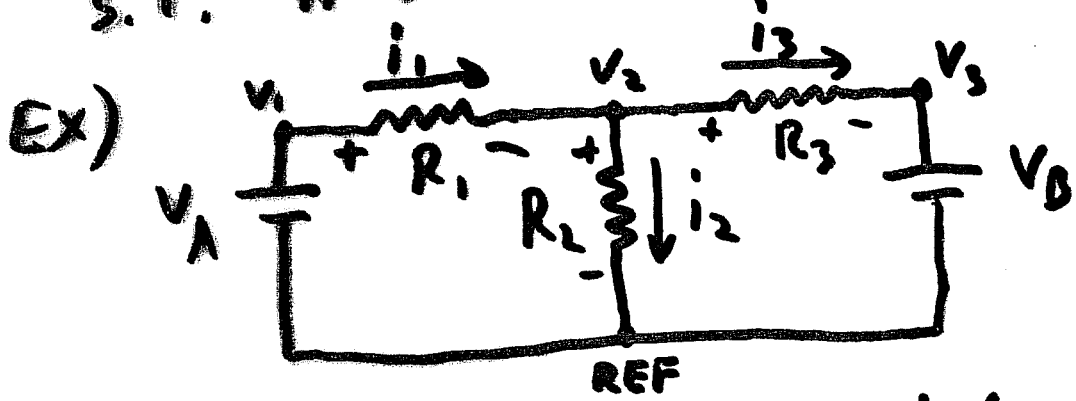- 1) Designate nodes on circuit
- 2) Assume currents flow to right & downward, and label resistors' polarities accordingly
- 3) using KVL & KCL, write equations expressing unknown i 's in terms of unknown V 's
 S.T. # OF EQN'S = # OF UNKNOWN'S. SOLVE FOR V 'S



BY INSPECTION: $V_1 = V_A$ & $V_3 = V_B$


$\Rightarrow V_2$ is only unknown

KCL: entering = leaving

$\Rightarrow \frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3}$. substitute

$\Rightarrow \frac{V_A - V_2}{R_1} = \frac{V_2}{R_2} + \frac{V_2 - V_B}{R_3}$

Node Analysis:

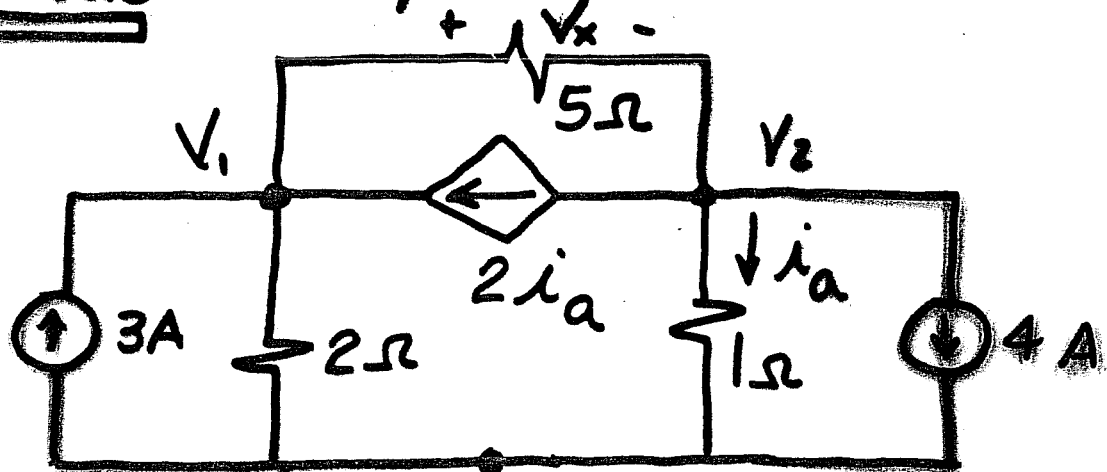

Ref.

Find V_x . ($V_x = V_1 - V_2$)

V_1	V_2	Sources
$(\frac{1}{2} + \frac{1}{5})$	$-\frac{1}{5}$	$3 + 2i_a$
$-\frac{1}{5}$	$(\frac{1}{5} + \frac{1}{1})$	$-2i_a - 4$

$$0.7 V_1 - 0.2 V_2 = 3 + 2i_a$$

$$-0.2 V_1 + 1.2 V_2 = -2i_a - 4$$


$$i_a = V_2 / 1$$

Mesh analysis

(6a)

- 1) Designate I_i around loops in a CW circular fashion.
- 2) Label polarities on resistors accordingly.
- 3) Use KVL's to write simultan. eq's
- 4) SOLVE FOR I_i 's


EX)

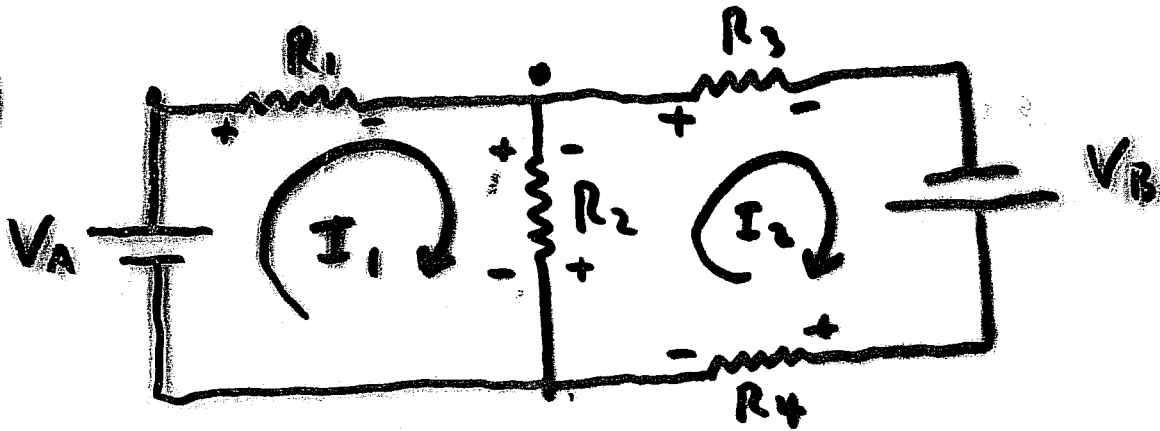

$$\text{KVL, LOOP 1: } I_1 R_1 + (I_1 - I_2) R_2 - V_A = 0$$


$$\text{KVL, LOOP 2: } I_2 R_3 - V_B + I_2 R_4 + (I_2 - I_1) R_2 = 0$$

Mesh Analysis:

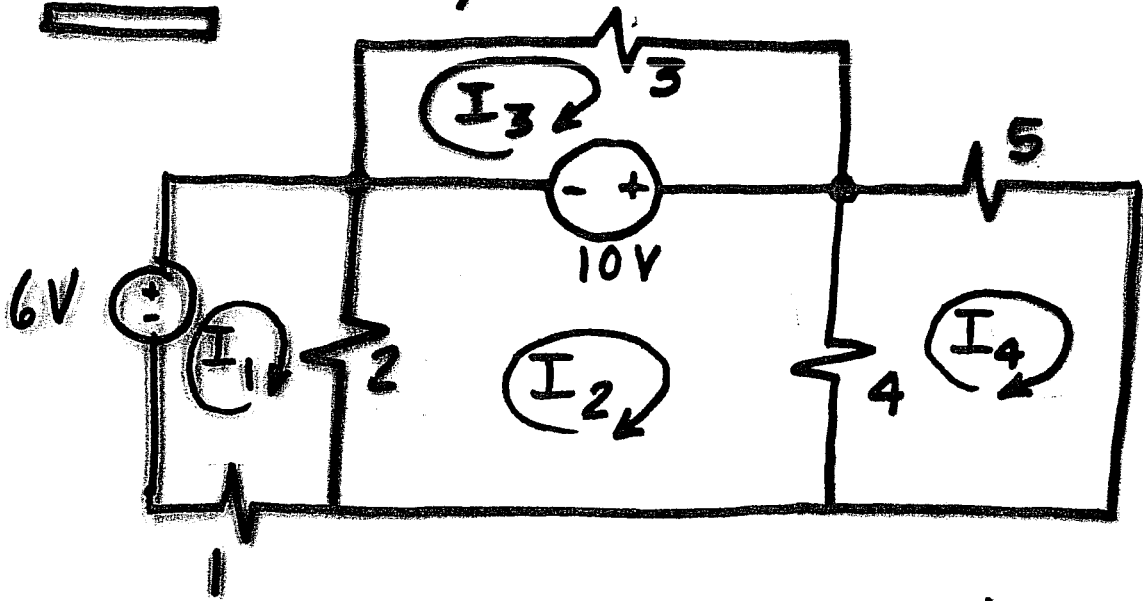


I_1	I_2	I_3	I_4	Sources
$2+1$	-2	0	0	6
-2	$2+4$	0	-4	10
0	0	3	0	-10
0	-4	0	$4+5$	0


Resistor Combinations :

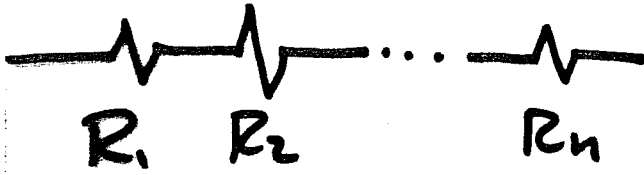



$$R_{eq} = R_1 + R_2 + \dots + R_n$$

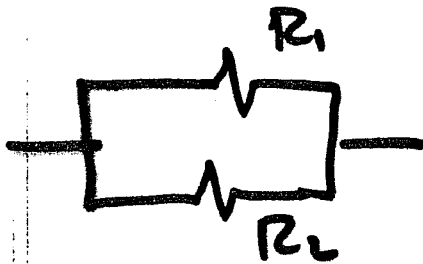

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

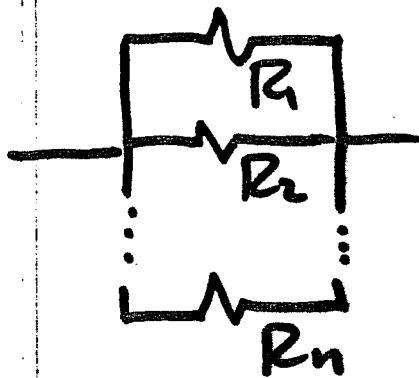
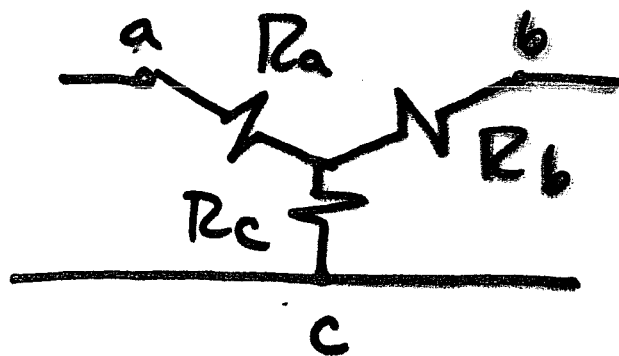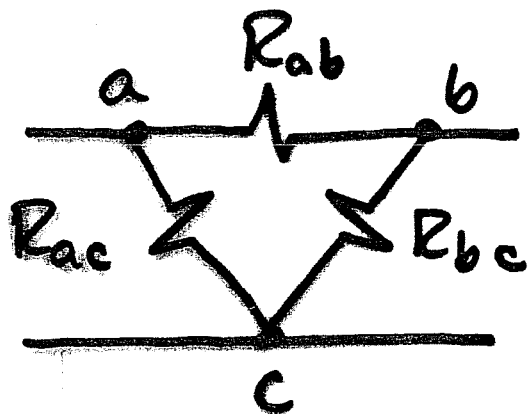
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$




$$R_a = \frac{R_{ac} R_{ab}}{R_{ac} + R_{bc} + R_{ab}}$$

$$R_{ac} = \frac{R_a R_c + R_b R_c + R_a R_b}{R_b}$$

$$R_x = \frac{\text{Product Adjacent}}{\Sigma}$$

$$R_{xy} = \frac{\Sigma \text{ Pairwise Products}}{\text{Opposite}}$$


Power:

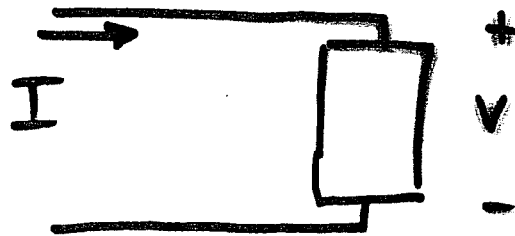

$$\underline{P_{\text{absorbed}}} = V I$$


If element is a source delivering energy to the rest of the circuit, I (or V) will be negative, and P_{absorbed} will be negative.

DEI

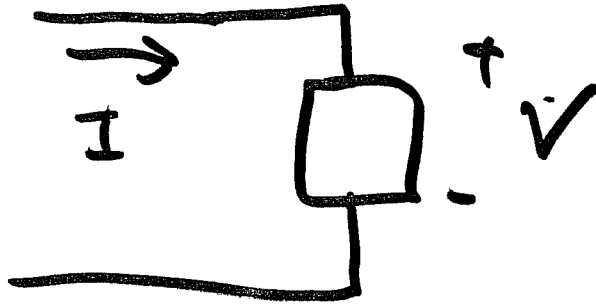


I	V	POWER
+	+	ABSORBED
+	-	DELIVERED
-	+	DELIVERED
-	-	ABSORBED

Thevenin Equivalent:

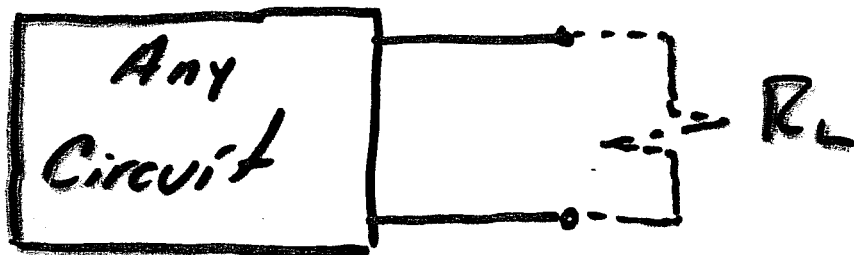

III

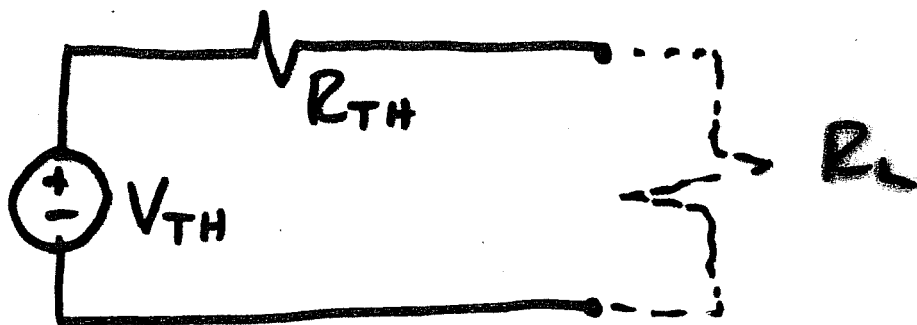

V_{TH} = Calculate open circuit V

R_{TH} = Turn off all sources


($V=0, I=0$) & measure R

(This works only if all sources are independent)

If dependent sources are present,

$$R_{TH} = \frac{V_{open\ circuit}}{I_{short\ circuit}}$$

Ex:

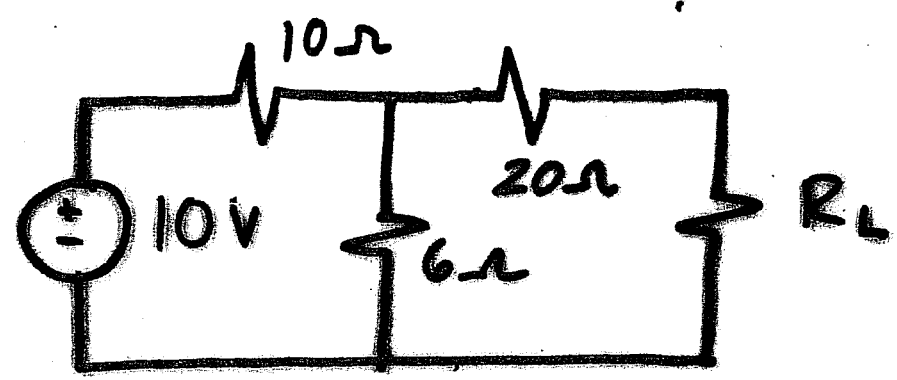


$$V_{TH} = \left(\frac{10}{10+6} \right) \cdot 6 = 3.75\text{ V}$$

$$R_{TH} = 20 + \frac{6 \cdot 10}{6+10}$$


$$= \underline{\underline{23.75\ \Omega}}$$

Maximum Power Transfer

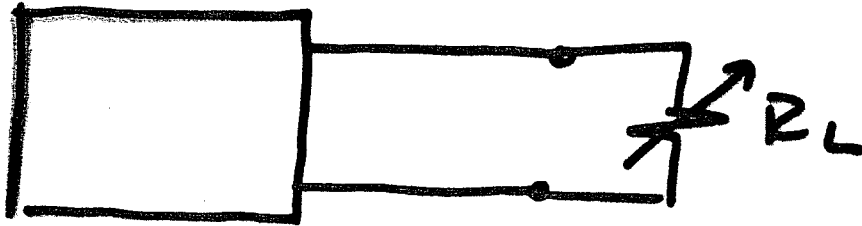


Maximum power is delivered to R_L if R_L is set equal to R_{TH} .

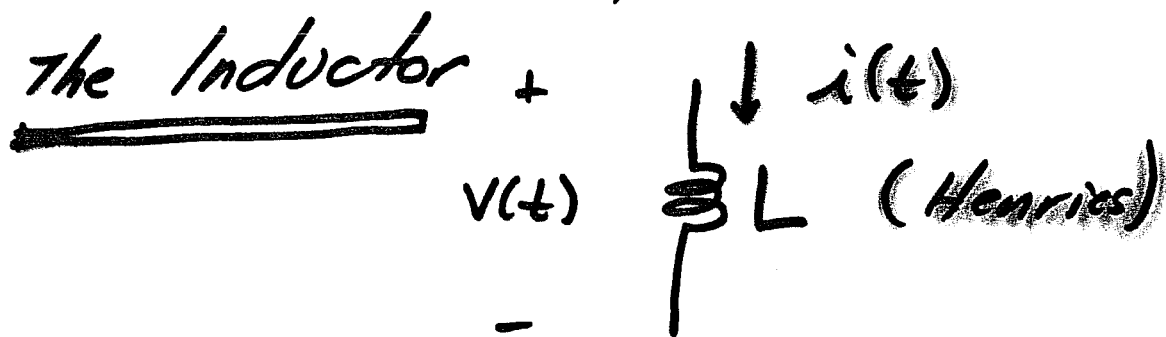For example of previous page, set R_L to 23.75Ω .



$$v(t) = L \frac{di(t)}{dt}$$
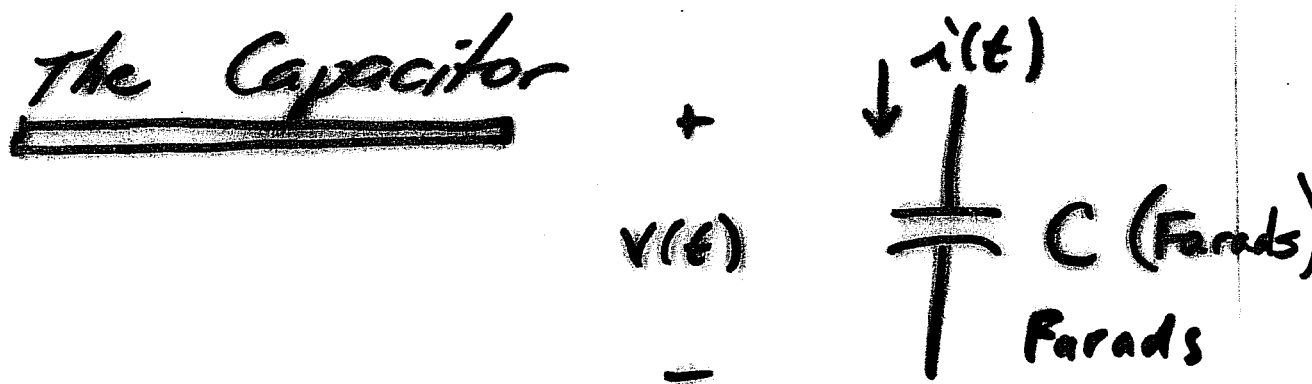
$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0)$$



$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

RL & RC Transients

For a network with R's, constant V and/or I sources, and one L or one C, the solution for any voltage or current is of the form :


$$x = A + B e^{-t/\tau}$$

where $\tau = R_{eq} C$ (CAP
CIR)

or $\tau = L / R_{eq}$ (IND
CIR)

∴ R_{eq} is resistance "seen" by L or C. (Thevanin's resistance)

Ex:

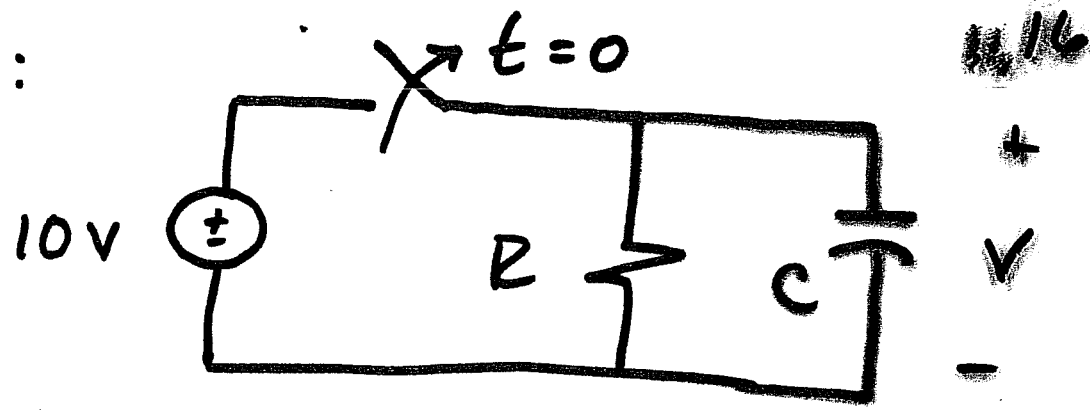


$$V(t) = A + B e^{-t/RC}$$

$$V(0) = 10 = A + B e^0 = A + B$$

$$V(\infty) = 0 = A$$

$$\therefore V(t) = 10 e^{-t/RC}$$


16a)

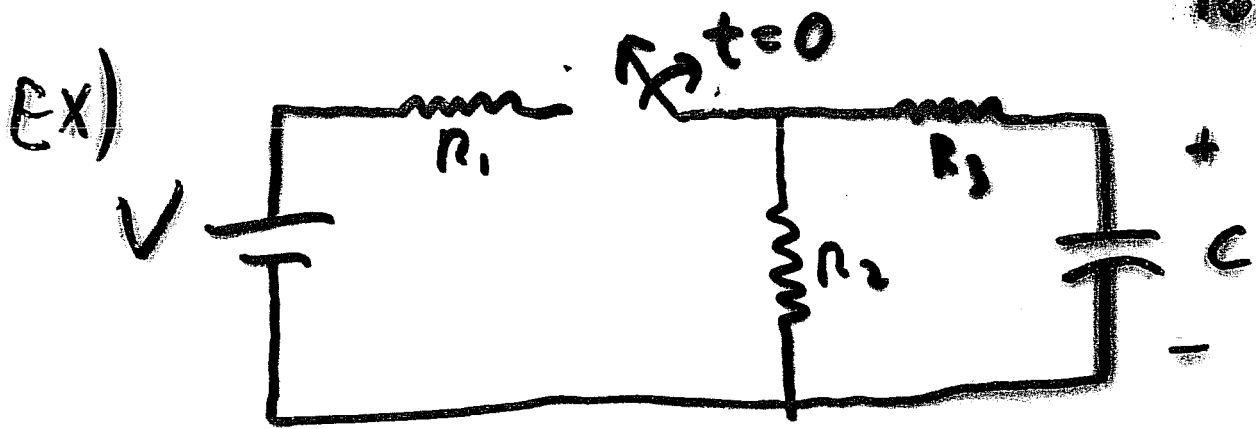

$$V_C(0^-) = \frac{V(R_2)}{R_1 + R_2} \quad \tau = C(R_1 + R_2)$$

$$V_C(t) = V_C(0^-) e^{-\frac{t}{C(R_1 + R_2)}}$$


EX)

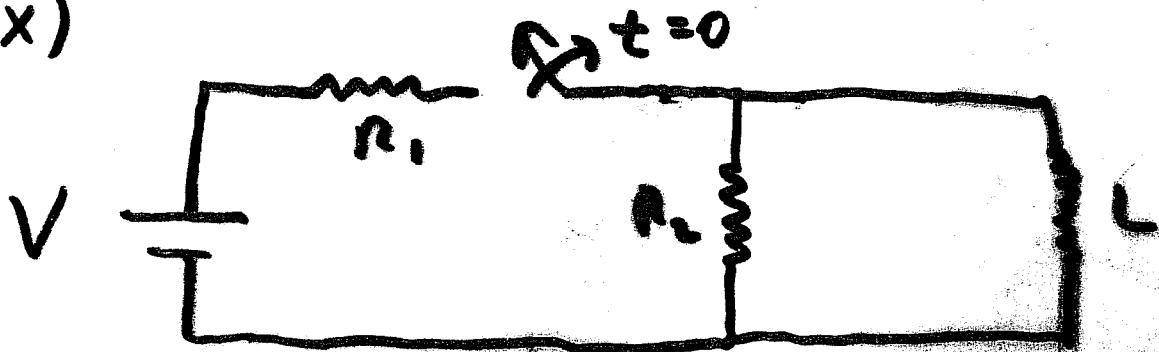

$$i_L(0^-) = \frac{V}{R_1} \quad (L \text{ ACTS LIKE SHORT})$$

$$\Rightarrow I_L(t) = i_L(0^-) e^{-\frac{t}{\tau}} ; \quad \tau = \frac{L}{R_2}$$

Ex:

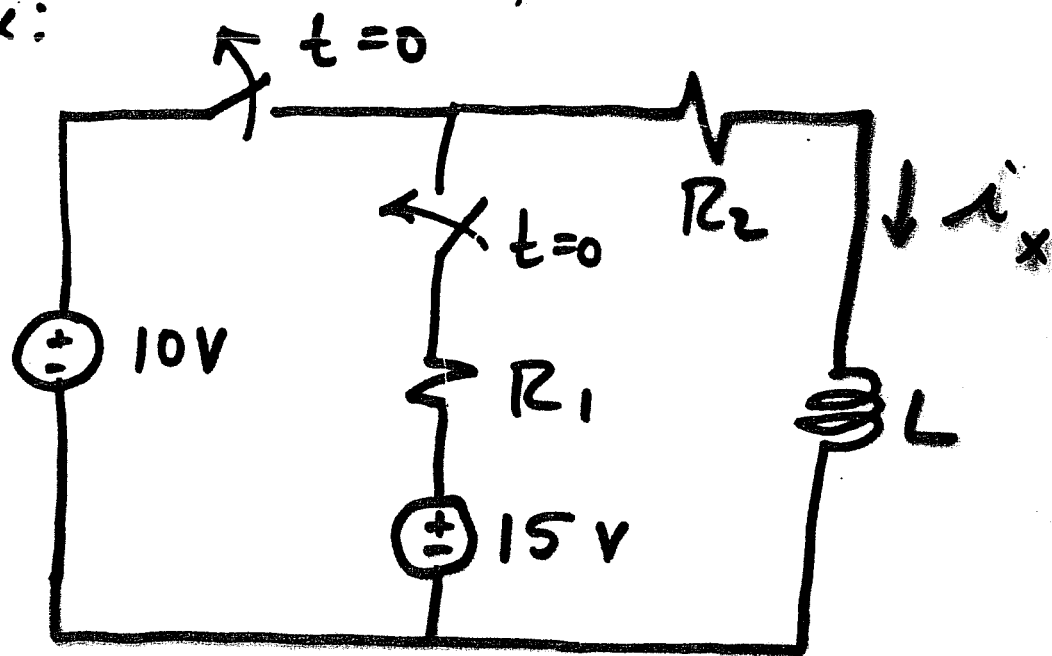

$$i_x(t) = A + B e^{-t/\tau}$$

$$i_x(0^-) = \cancel{A} + B = 10/R_2$$

$$i_x(\infty) = A = 15/(R_1 + R_2)$$

$$\tau = L / (R_1 + R_2)$$

Note: From $v_L = L di/dt$

$\therefore i_C = C dv/dt$, v_C and i_L

cannot change instantaneously.

$$\therefore i_x(0^+) = i_x(0^-)$$

When currents and voltages are constant, energy stored in C's & L's is given by:

$$E_L = \frac{1}{2} L i_L^2$$

$$E_C = \frac{1}{2} C v_C^2$$