

Electrical Science

EIT Review

Session 2

Phasors


Impedance

Resonance

Power & RMS units

Complex Power

Phasors

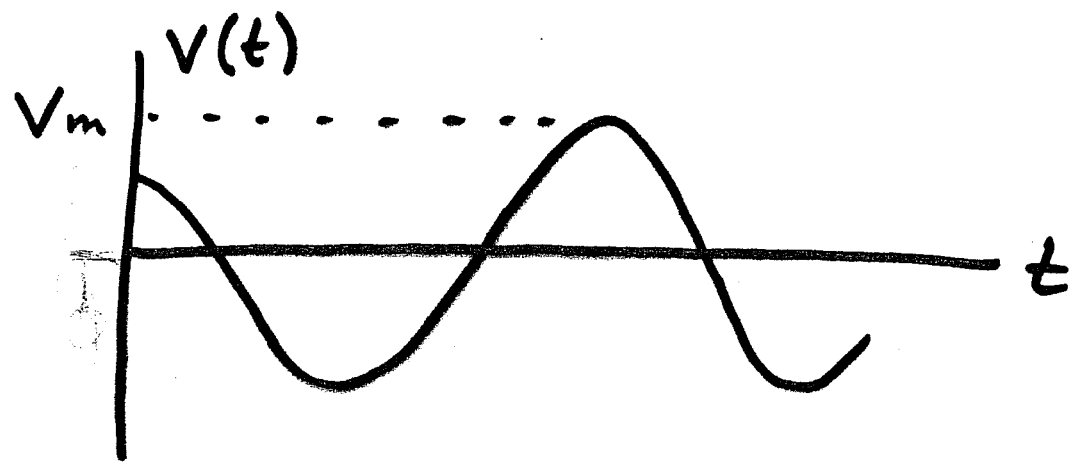


$$v(t) = V_m \cos(\omega t + \phi)$$


$$\omega \triangleq 2\pi f$$

UNITS: $\frac{\text{RAD}}{\text{s}}$

$$\bar{V} = V_m \angle \phi$$

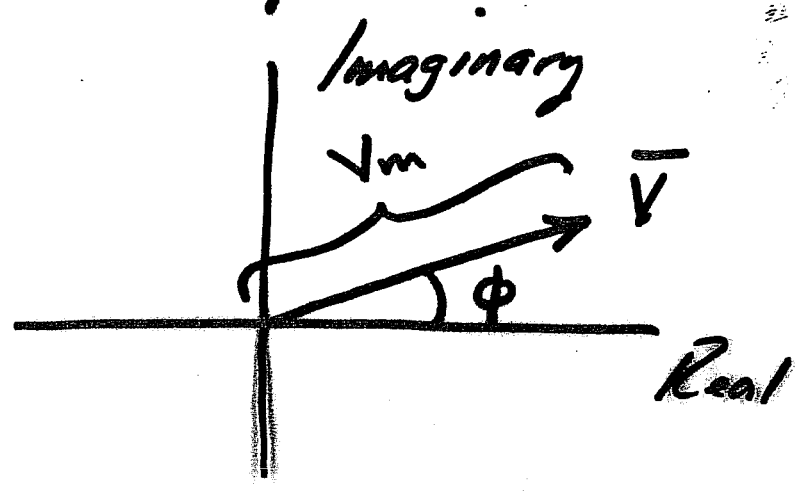

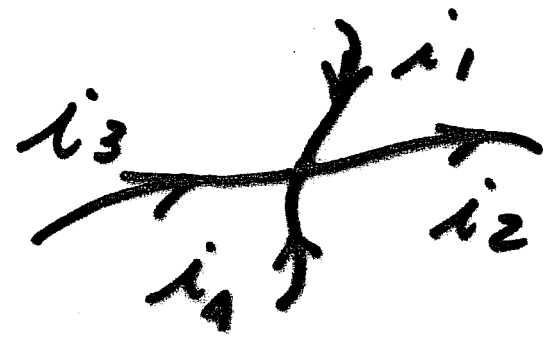Phasors are combined using complex arithmetic.




$$i_1 = 5 \cos(5t + 45^\circ)$$

$$i_2 = ? = i_1 + i_3 + i_4 \text{ (by KCL)}$$


$$i_3 = 7 \cos(5t - 135^\circ)$$

$$i_4 = 3 \cos 5t$$

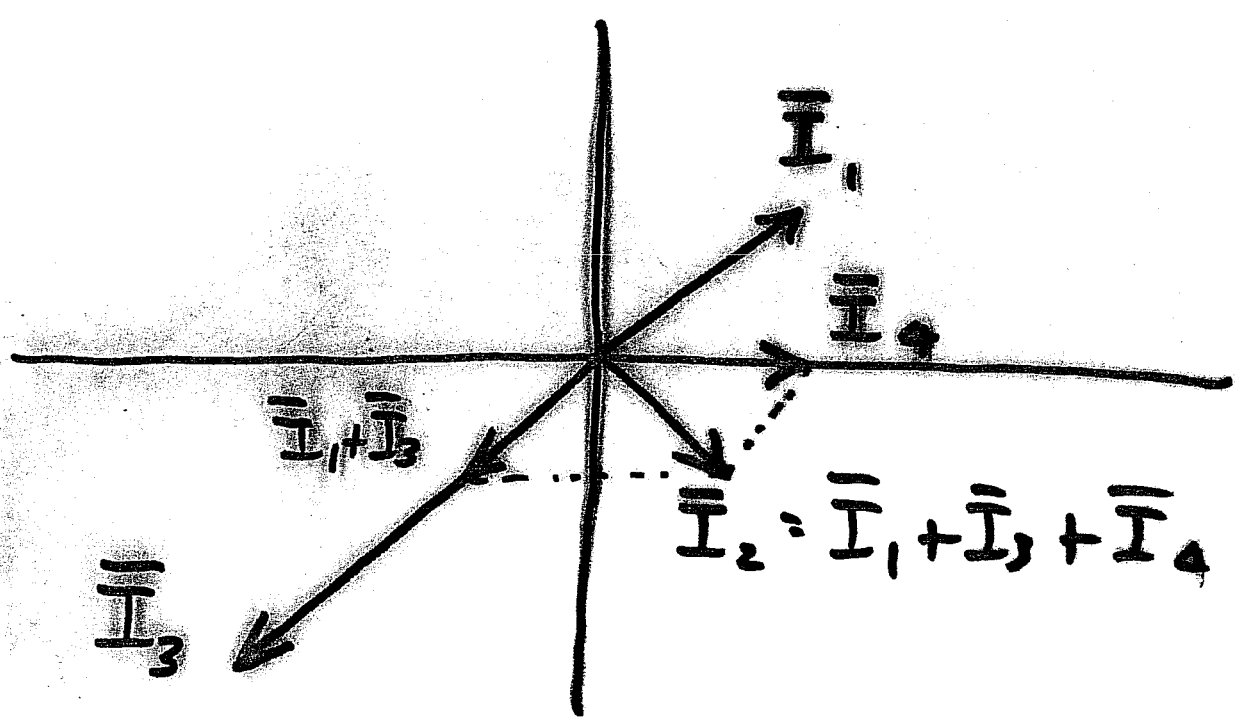


Impedance (Sinusoidal analysis only) 4


$$\bar{I} = \bar{V} / Z \quad (\text{Ohm's law})$$


 $Z = R$



 $Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$


 $Z = j\omega L$

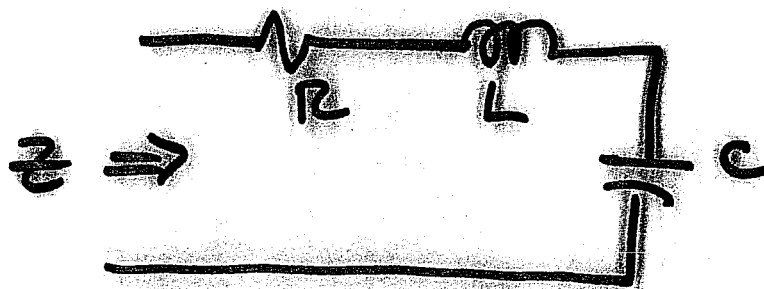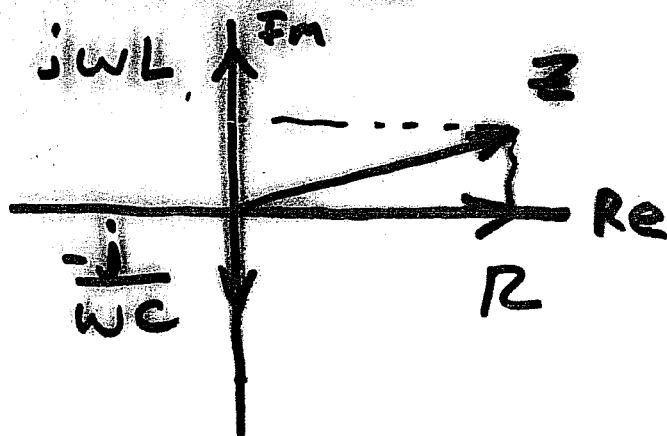
$\omega \triangleq 2\pi f$
 UNITS: $\frac{\text{RAD}}{\text{s}}$



$$Z = R + j\omega L + \frac{1}{j\omega C}$$



Ex:

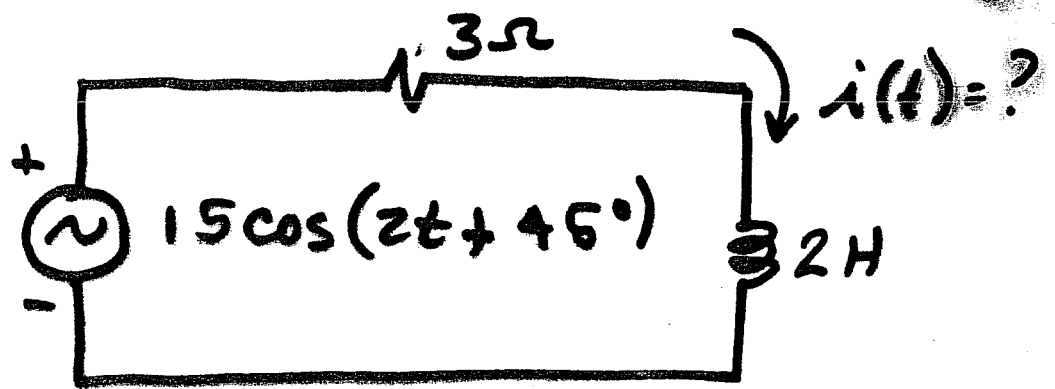

$$\bar{V} = 15 \angle 45^\circ$$


$$Z = 3 + j(2)(2) = 3 + j4 = 5 \angle 53.1^\circ$$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{15 \angle 45^\circ}{5 \angle 53.1^\circ}$$


$$\bar{I} = 3 \angle -8.1^\circ$$

$$i(t) = 3 \cos(2t - 8.1^\circ)$$

Z's combine like R's :

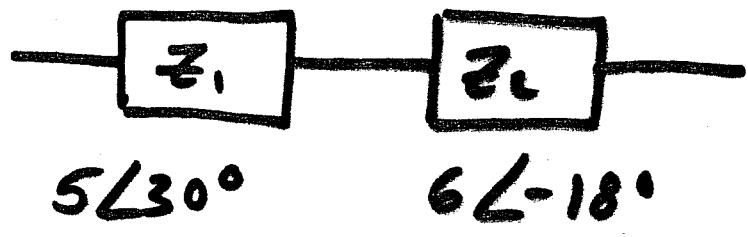
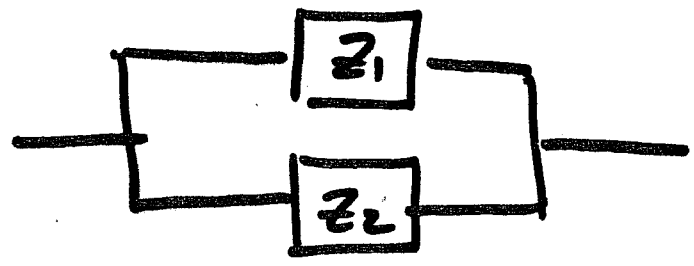
$$Z_{eq} = 5\angle 30^\circ + 6\angle -18^\circ$$





$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

lots of complex arithmetic

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$

Resonance

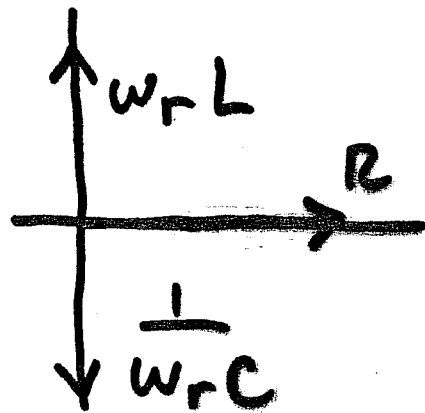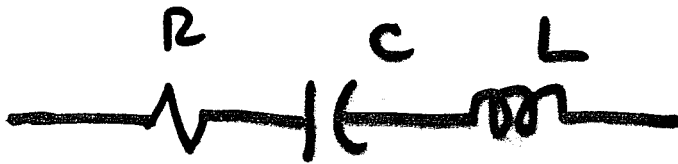

At ω such that


$$\omega_r L = \frac{1}{\omega_r C}, \quad z_L = z_C$$

C & L z 's cancel

leaving only R .

$$\omega_r = \frac{1}{\sqrt{LC}}$$

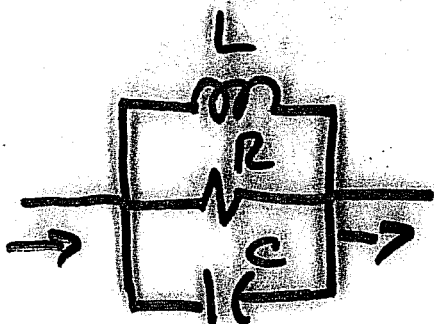If elements are in parallel,
 z_L & z_C combine to form an
infinite impedance, leaving only R !



$$\text{At } \omega_r = \frac{1}{\sqrt{LC}},$$

$$z = R.$$

Power & RMS Units

$p(t) = v(t) i(t)$ (instantaneous power)

Average Power = $\int p(t) dt$ over one cycle.

$= |\bar{V}| |\bar{I}| \cos \theta$

where

\bar{V} = voltage (in rms units)

\bar{I} = current (in rms units)


θ = ϕ between \bar{V} & \bar{I} .

RMS units are defined as:

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

For sinusoids: $V_{rms} = \frac{V_{max}}{\sqrt{2}}$

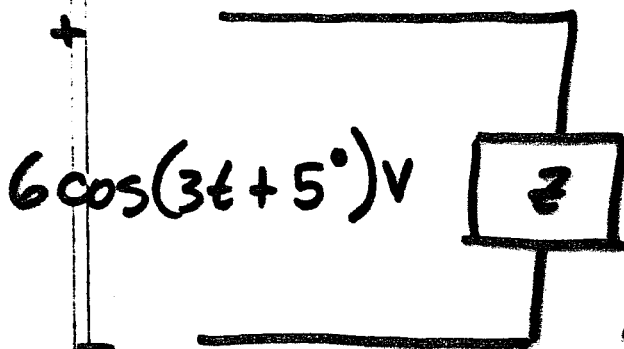For other waveforms,
you must carry out the
calculation.



Find average power delivered to Z .

$$Z = 2 \angle -15^\circ$$

$$\bar{V}_{rms} = \frac{6}{\sqrt{2}} \angle 5^\circ$$

$$\bar{I}_{rms} = \frac{\bar{V}_{rms}}{Z} = \frac{\frac{6}{\sqrt{2}} \angle 5^\circ}{2 \angle -15^\circ}$$

$$\bar{I}_{rms} = \frac{3}{\sqrt{2}} \angle 20^\circ$$

$$P_{ave} = \left(\frac{6}{\sqrt{2}}\right) \left(\frac{3}{\sqrt{2}}\right) \cos(20^\circ - 5^\circ)$$

$$P_{ave} = \frac{18}{2} \cos(15^\circ)$$

Notes:

- ① Don't worry about whether to use + or - θ , since $\cos(\theta) = \cos(-\theta)$
- ② $\cos \theta$ is called the Power Factor.
- ③ If you are asked for the power at any given time, you must use $p(t) = v(t)i(t)$.

Ex: For previous problem,
find power being delivered
to Z at t = 0.1 sec.

$$v(t) = 6 \cos(3t + 5^\circ)$$

$$i(t) = 3 \cos(3t + 20^\circ)$$

$$p(t) = 18 \cos(3t + 5^\circ) \cos(3t + 20^\circ)$$


$$p(t) = 18 \cos(.3 + 5^\circ) \cos(.3 + 20^\circ)$$

Careful!!

radians

degrees

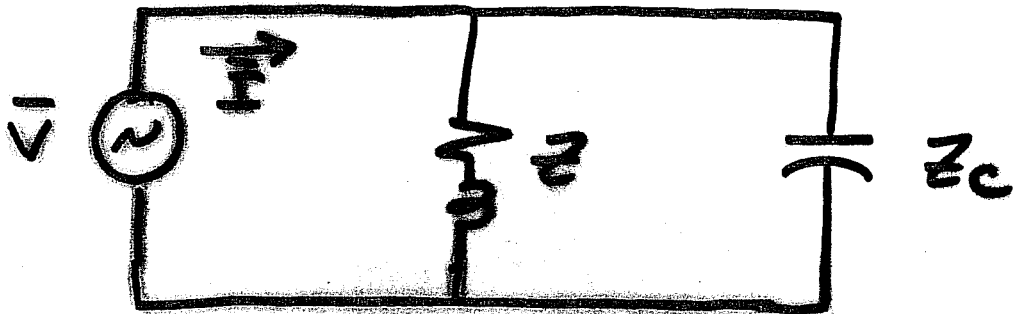If the ϕ of Z is positive (inductive) the current lags the voltage, and the power factor is described as lagging. The standard problem is :




How much Z_c is needed to make \bar{I} and \bar{V} in phase (1.0 power factor)?

Ex:

A single phase inductive load takes 50 kVA at 0.6 p.f. lagging. The amount of capacitance (in kilovars) needed to improve the power factor to unity is:

Sol'n:

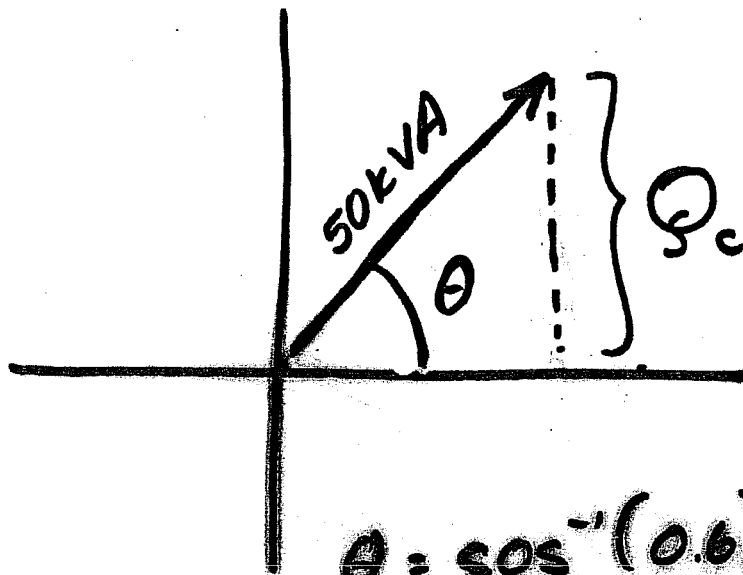

$$Q_c = S \sin \theta$$

$$\theta = \cos^{-1}(0.6) \\ = 53.1^\circ$$

$$Q_c = (50 \text{ kVA}) \sin(53.1^\circ)$$

$$Q_c = 40 \text{ kVARs}$$